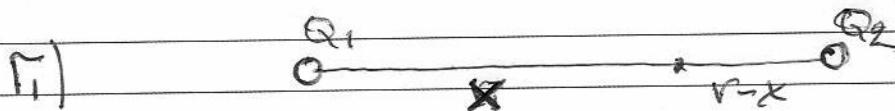


# Applikationen OperativW. 2016-17

A<sub>1</sub>-8, A<sub>2</sub>-8, A<sub>3</sub>-5, A<sub>4</sub>-6, A<sub>5</sub>-1, Σ, Λ, Λ, Σ.

$$B_1 - 8 \quad \Delta \text{G} \cdot k \frac{2Q}{r_1^2} = k \frac{Q}{r_2^2} \Rightarrow \frac{r_1^2}{r_2^2} = 2 \Rightarrow \frac{r_1}{r_2} = \sqrt{2}$$

$$B_2 - 6 \quad \Delta \text{G} \cdot V_H = \Sigma - I \cdot r = \Sigma - \frac{V_H}{R} r \Rightarrow 8 = 10 - \frac{8}{8} r \Rightarrow \\ \Rightarrow r = 20.$$



$$k \frac{Q_1}{x^2} = k \frac{Q_2}{(r-x)^2} \Rightarrow \left(\frac{r-x}{x}\right)^2 = \frac{Q_2}{Q_1} \Rightarrow \frac{16-x}{x} = \sqrt{q} \Rightarrow \\ 16-x = 3x \Rightarrow x = 4 \text{ cm}.$$

$$\Gamma_2). \quad V = k \frac{Q_1}{x} + k \frac{Q_2}{r-x} = q \cdot 10^9 \left( \frac{2 \cdot 10^{-6}}{4 \cdot 10^{-2}} + \frac{18 \cdot 10^{-6}}{12 \cdot 10^{-2}} \right) \Rightarrow \\ V = q \cdot 10^9 (0,5 + 1,5) \cdot 10^{-4} \Rightarrow V = 18 \cdot 10^5 \text{ Volt}.$$

$$\Gamma_3). \quad W = q(V - V_0) = q \cdot 10^{-6} \cdot 18 \cdot 10^5 = 3,6 \text{ Joule}$$

$$\Delta 1). \quad I = \frac{\Sigma}{R_{\text{ext}} + r} = \frac{12}{6} = 2 \text{ A}, \quad V_H = \Sigma - I r = 12 - 2 = 10 \text{ V}.$$

$$\Delta 2). \quad V_1 = I R_1 = 2 \cdot 2 = 4 \text{ V}, \quad V_2 = I R_2 = 2 \cdot 3 = 6 \text{ V}.$$

$$\Delta 3). \quad P_H = \Sigma \cdot I = 12 \cdot 2 = 24 \text{ W}.$$

$$P_1 = I^2 R_1 = 4 \cdot 2 = 8 \text{ W}, \quad P_2 = I^2 \cdot R_2 = 4 \cdot 3 = 12 \text{ W}$$

$$P_r = I^2 \cdot r = 4 \text{ W}.$$